

# **CSE260 Lab Report**

**Experiment Name: Familiarization of Fundamental Logic Gates**

**Submitted by**

**Name: Shabab Abdullah**

**ID: 20301005**

**Section: 09**

**Date: 4 July, 2021**

Name of the experiment:

Familiarization of Fundamental Logic Gates.

Objective:

To get familiarized with fundamental logic gates and demonstrate the input output relationship of 2-input AND (IC-7408) OR (IC-7432) and NOT (IC-7404) gates by construction constructing their truth tables.

To get familiarized with other logic gates like NAND (IC-7403) NOR (IC-7402), X-OR (IC-7486) and X-NOR (IC-74266).

P.T.O



## Required Components and Equipments:

1. AND (IC- 7408)

2. OR (IC- 7432)

3. NOT (IC- 7404)

4. NAND (IC- 7400)

5. NOR (IC- 7402)

6. X-NOR (IC- 74266)

7. X-OR (IC- 7486)

8. Logic Probe (Big)

9. Logic State.

10. Power.


11. Volt Meter.

12. Resistance.


13. Ground.



VCC +5

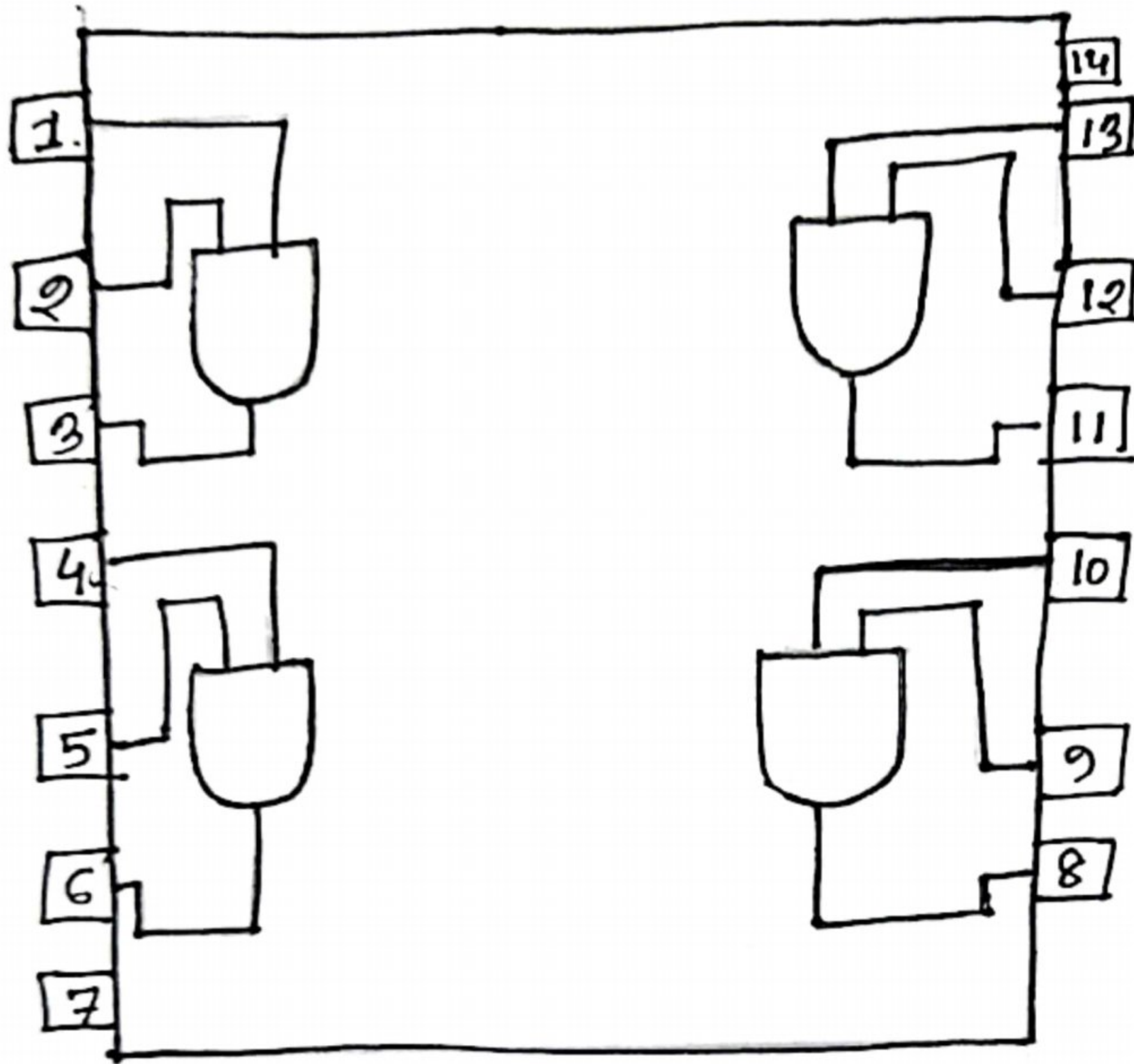


Pin Layout of 7408

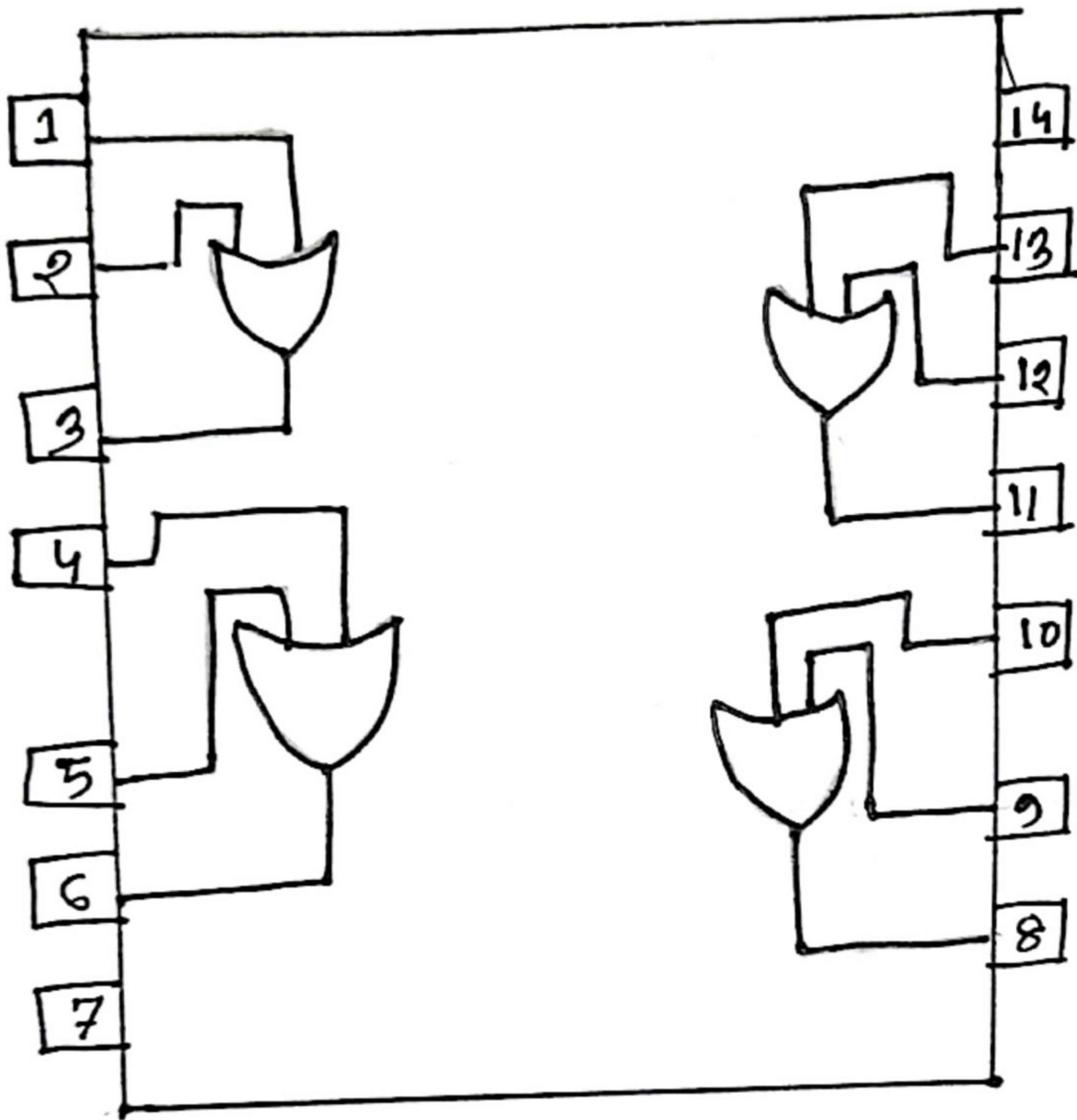


Pin layout of 7432



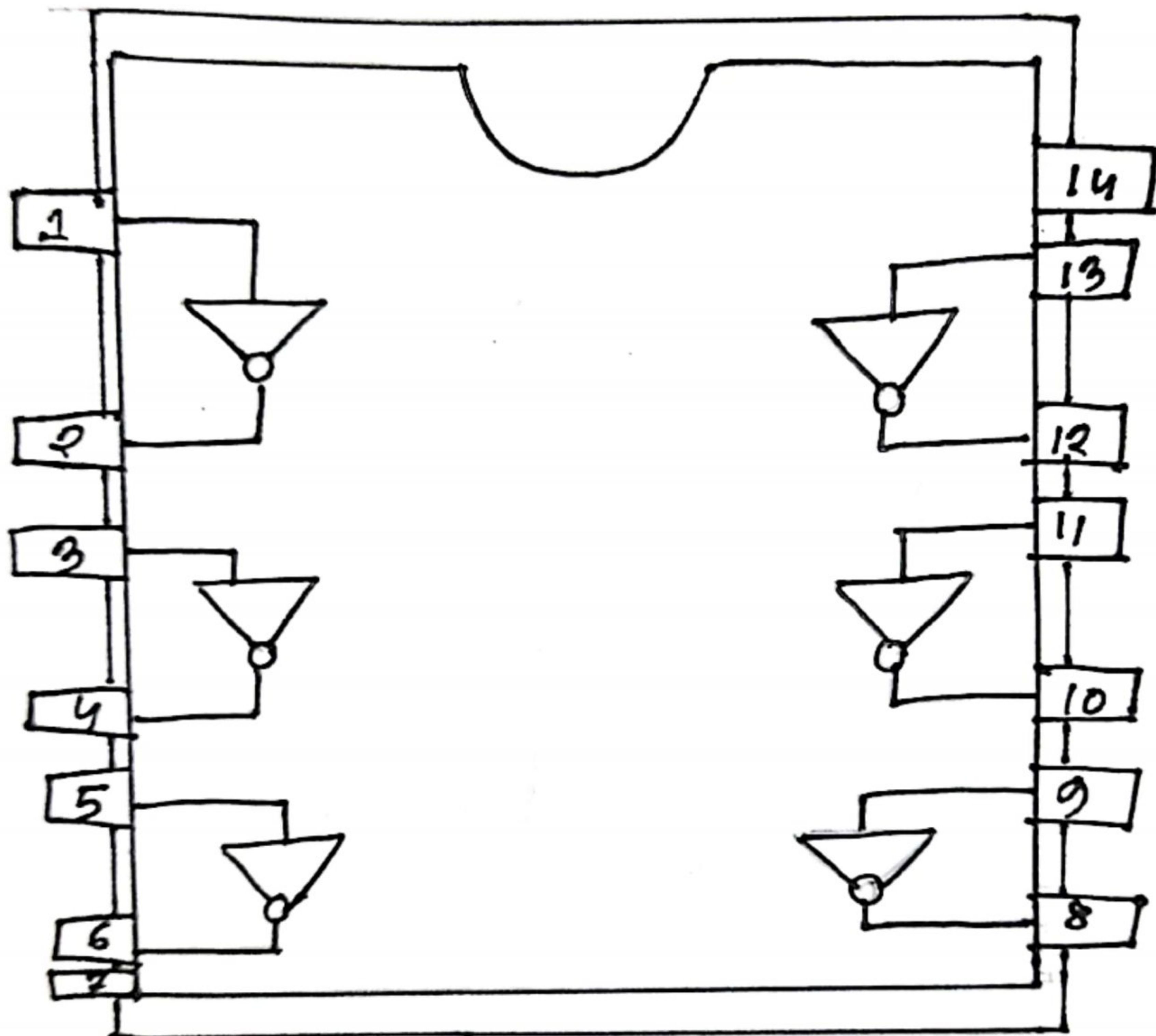


Pin Layout of 7404

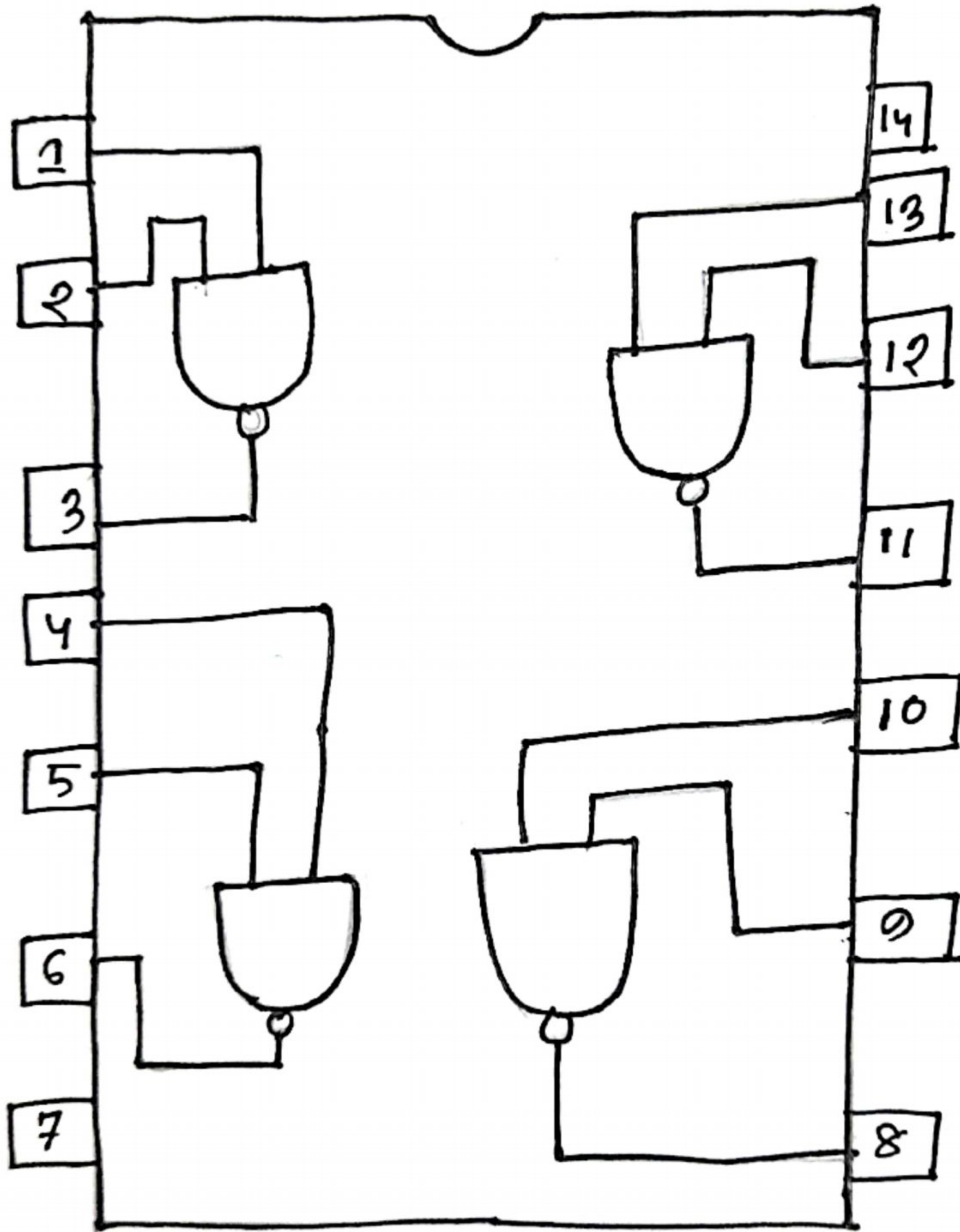


Pin Layout of 7400




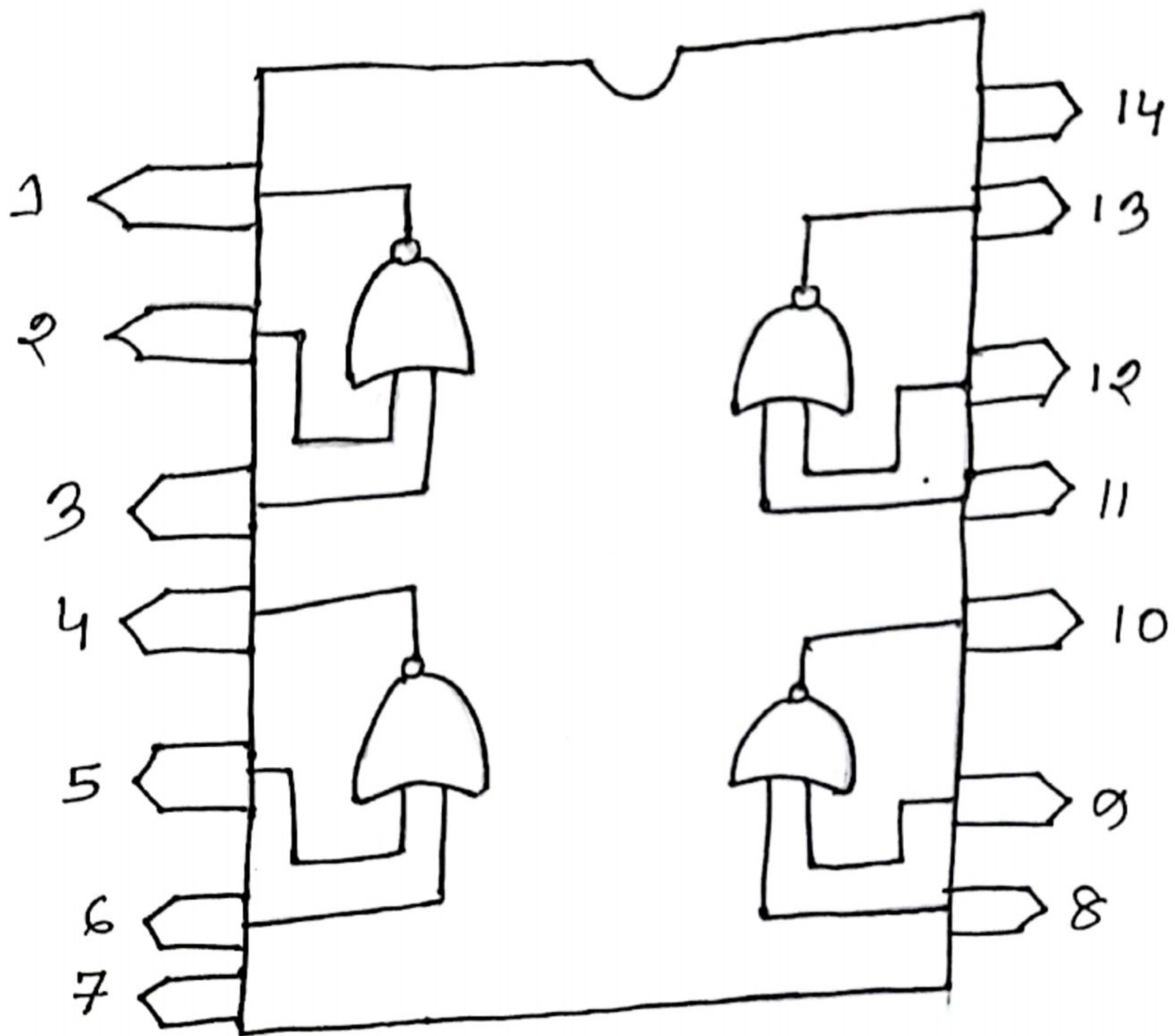



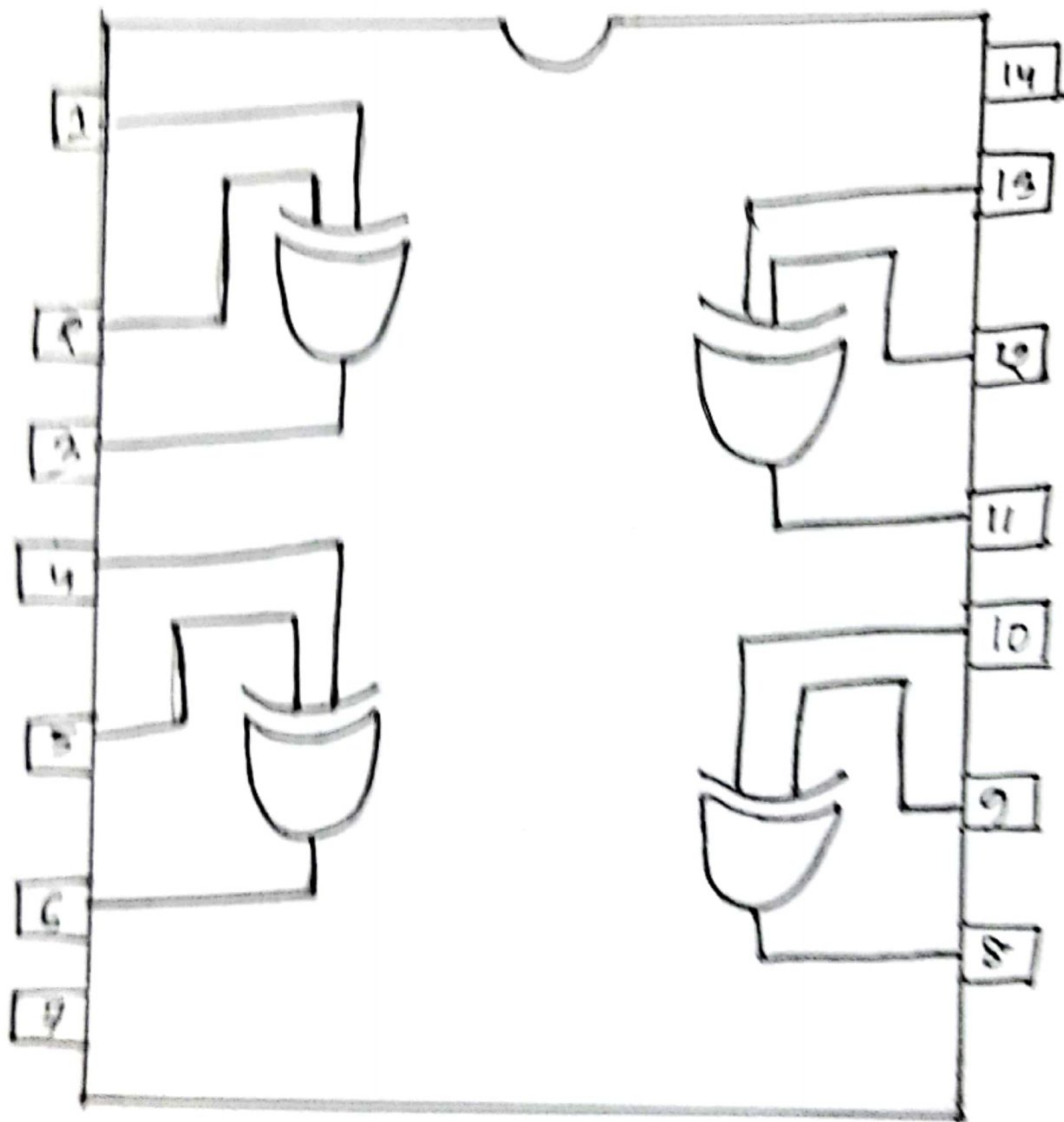

Pin layout of 7486

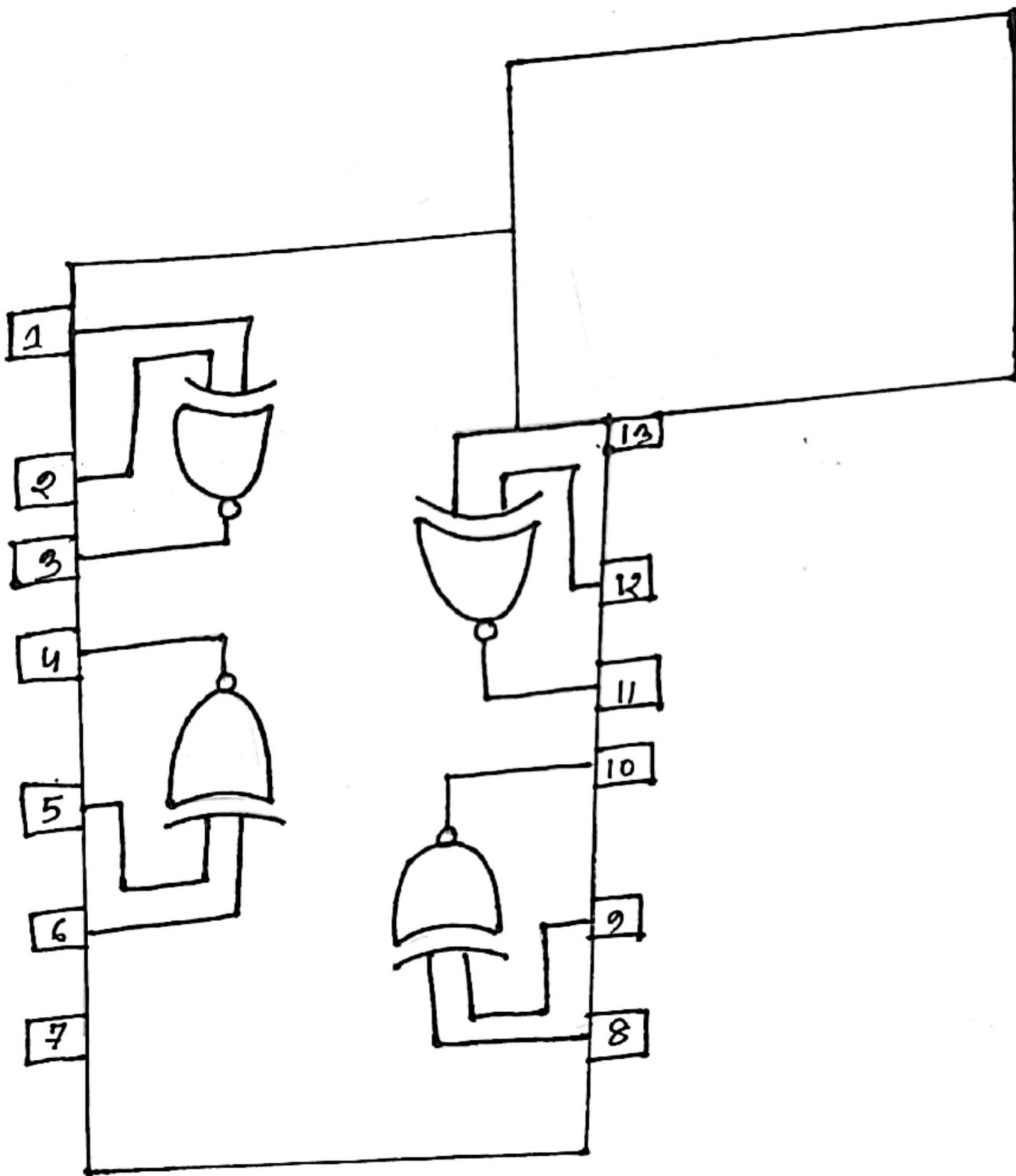


Pin Layout of 74266



## Truth Table :-

i) Truth table of AND gate:-

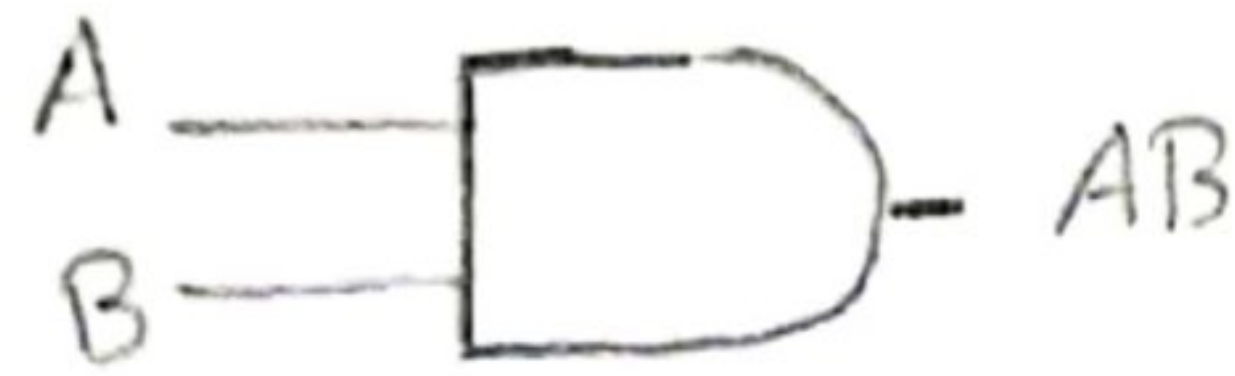

Input		Output
A	B	AB
0	0	0
0	1	0
1	0	0
1	1	1

ii) Truth table of OR gate:-



Input		Output
A	B	A+B
0	0	0
0	1	1
1	0	1
1	1	1



iii) Truth Table of NOT gate :-



A	A'
0	1
1	0


iv) Truth Table of XOR gate :-



Input		Output
A	B	$A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0




v) Truth table of X-NOR gate:-

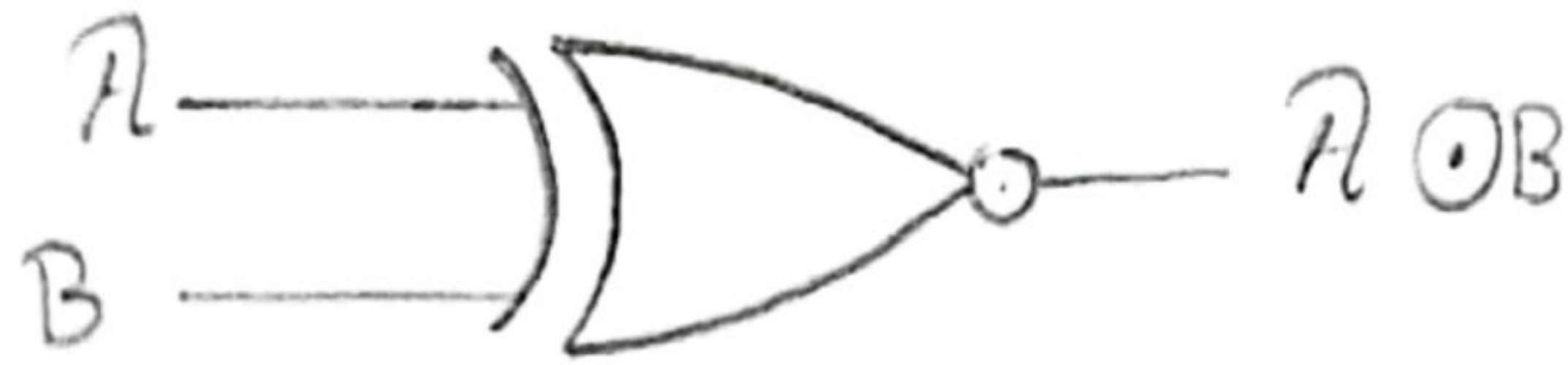

Input		Output
A	B	$A \odot B$
0	0	1
0	1	0
1	0	0
1	1	1

vi) Truth table of NAND gate:-

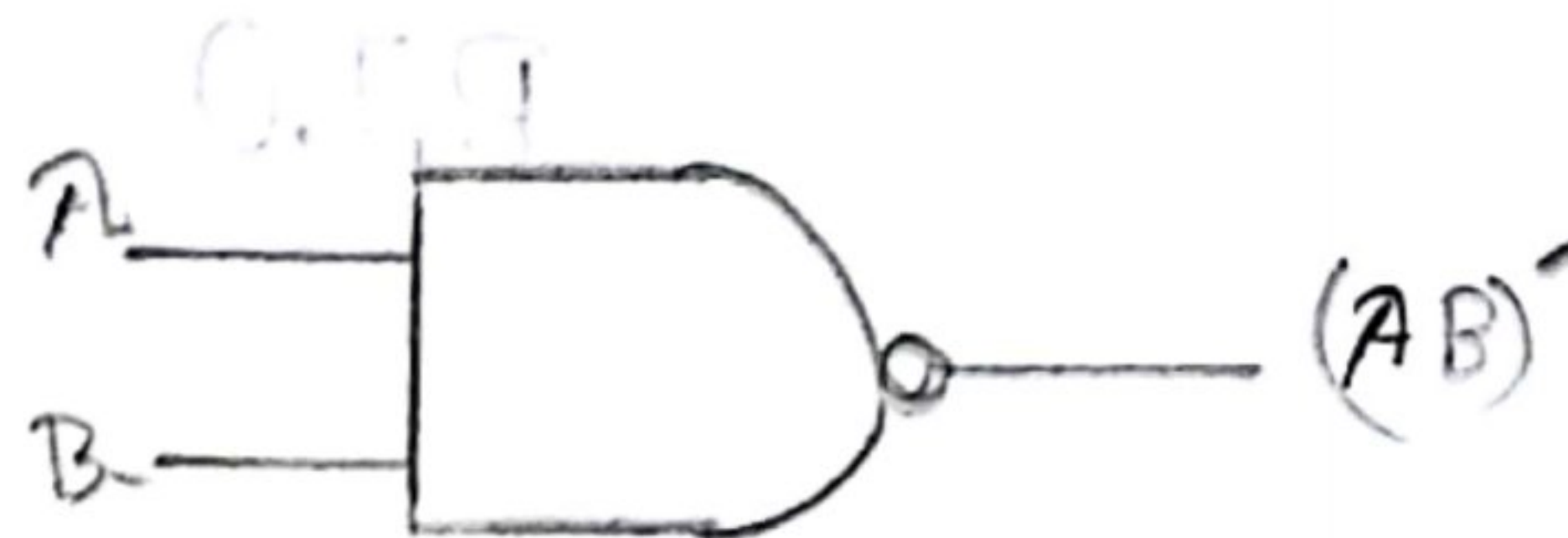

Input		Output
A	B	$(AB)'$
0	0	1
0	1	
1	0	
1	1	



vii) Truth table of NOR-gate:-



Input		Output
A	B	$(A+B)'$
0	0	1
0	1	0
1	0	0
1	1	0

P.T.O



## Discussion 8-

Throughout this exercise, we were introduced to the fundamental logic gates, which consist of two inputs and a single output. We used an online simulator called Proteus to get a better understanding of how they work. All of the logic gates have two inputs, which is typical for logic gates in general. Basic logic gates ~~have two~~ are used in a wide range of applications, many of which are familiar to us.